

Audio Electronics

I. Transformers

a. Intro

- i. Two or more inductors placed back to back to each other wrapped around a core.
- ii. Magnetic field created when AC current passes through inductor, and visa versa (Faraday's Law)
- iii. When two inductors are placed next to each other, a magnetic field in one will generate current in the other
- iv. Input is primary coil, output is secondary coil
- v. Number of turns in each inductor determines the strength of the field in the first and the current in the second.

b. Isolation Transformers

- i. No physical contact is made with transformers, preventing ground loops.
- ii. Ground loops occur when there is more than one path to ground and electrons circle around the loop instead of going to ground, leading to noise.
- iii. Important in studios with lots of gear, or racked devices connecting to ground through the chassis
- iv. Transformers used on inputs and outputs of these devices to physically isolate them
- v. Usually have a 1:1 turns ratio
- vi. More expensive isolation transformers need to be used in order to pass all audible frequencies, however simple isolation transformers can be used for debugging.
- vii. Faraday's Law only applies for AC. DC currents won't be passed with transformers, making them DC blockers.

c. Input/Output Phase Relationship

- i. Direction of turns in the inductor determines if the input and output are in or out of phase
- ii. Dot convention used where transformers are marked to know whether or not the output is in phase
- iii. Phase not always relevant, assumed to be in phase if unmarked

d. Input/Output Amplitude Relationships

- i. The **turns ratio** is primary : secondary coils and this determines input/output amplitude.
- ii. Relationship: $a = n_p/n_s = V_p/V_s = I_s/I_p$
- iii. Can be used for simple calculations
- iv. Some power is realistically lost to heat. However, power can never increase.

e. Step up and Step Down

- i. Maximum voltage is ideal for audio gear, transformers can be used to maximize voltage.
- ii. "stepping up" voltage, **step up** transformer
- iii. Reducing voltage is a **step down** transformer
- iv. There is a limit to how much voltage can be amplified with transformers.
- v. When increased current no longer increases the magnetic field, coil is **saturated**.
- vi. Driving coil past saturation point leads to distortion
- vii. Voltage or current shouldn't be amplified more than +25dB

- viii. Often used in high power amplifiers in cars
 - ix. Step down transformers used convert electricity at wall into DC voltage more suitable for gear
 - f. Impedance Adjusting
 - i. Most common use in audio is adjusting impedance, especially between mic and pre amp
 - ii. Amps designed to deliver to high impedance and loudspeakers have a low load impedance.
 - iii. Transformer used to transform load impedance to satisfy both devices.
 - iv. This is due to **load reflection**, the basic way transformers operate
 - v. Impedance between source and load always adjusted when using transformers
 - vi. $N_p/n_s = V_p/V_s = I_s/I_p = \sqrt{Z_p}/\sqrt{Z_L}$
 - vii. Use this to calculate turns ratio necessary for adjusting impedance a certain amount
 - g. Balanced/Unbalanced Conversion
 - i. Make use of multiple coil transformers
 - ii. In multiple coil transformers, there are multiple turns ratios, if ratios identical, primary will appear at each of the secondaries with same amplitude
 - iii. Splitting transformer has on primary and two secondary coils, used in DI boxes to convert unbalanced to balanced signal
 - iv. Splitter can be reversed, transformer based DI boxes are useful because they work in both directions.
 - v. Placing a center tap on the transformer allows it to serve balanced/unbalanced use or that of a simple transformer
 - vi. Multi-tapping a secondary transformer also allows for connection to different load impedances
 - h. Bandwidth
 - i. Parasitic capacitances and inductances form between coils and have a band pass response on the frequency
 - ii. Cheap transformers can only pass about 80Hz to 3kHz, while high quality ones can pass all audible frequencies
 - i. CMRR
 - i. Transformers used for mic preamps to convert signal and cancel out noise
 - ii. Quality of noise subtraction is specified by Common Mode Rejection Mode
 - iii. Applying same signal to each input is known as common mode signal
 - iv. Rejection ratio given in db, higher value, better the subtraction.
- II. The Op-Amp
- a. Intro
 - i. Three types of amplification: voltage, current, and power
 - ii. Mic preamps, effects, and synths are based upon voltage amplification, done through op amp
 - iii. Op amps are mostly voltage amplification
 - iv. Negative feedback often used to stabilize signal and give wider bandwidth, giving better fidelity for less amplification
 - v. Op amp contains voltage amplifier, has high input impedance and low output impedance
 - vi. Acts as a high impedance load and low impedance source

- vii. Amplifies voltage and current with external power
 - viii. 2 input pins and one output (**differential input**)
 - ix. Packaged in 8 pin assembly called dual inline package, with two op amps inside sharing a power supply
- b. Comparator
- i. Op amps can be open or closed loop
 - ii. Open loop mode when two sources applied and a load
 - iii. If two sources connected to each pin, equation is: $V_{out} = (+V_a - V_b)(\text{Open loop gain})$
 - iv. Open loop gain often in vicinity of 10,000 to 1,000,000
 - v. Despite large gain, voltage cannot exceed voltage of “rails” and will **rail out** if output tries to exceed supply
 - vi. This circuit is basically used to return a positive or negative number based on which source is greater
 - vii. A use for this is as a gate
 - viii. This is one of the few circuits where output will exceed the supply
- c. Closed Loop Mode Amplifiers
- i. Op Amps much more useful when feedback loops used
 - ii. Negative feedback is when output is fed back to inverting input and positive feedback is when output is fed back to non inverting input
 - iii. Amplifiers/attenuators use negative feedback. Oscillators use positive feedback.
 - iv. Exception is a filter using positive feedback and 100% negative feedback to stabilize amp
- d. Inverting Negative Feedback
- i. When positive terminal is connected to ground and input connected to negative terminal, with feedback to the negative terminal equation is: $V_{out} = -V_{in}(R_f/R_i)$
 - ii. Voltage amplified when $R_f > R_i$, attenuated when $R_f < R_i$, unity when 1:1.
 - iii. Resistors larger than 100K can cause amp to become unstable as it approaches open loop gain mode
 - iv. Feedback stabilizes output to lower the gain
 - v. In ideal op amp, no current flows into either terminal and the difference in input voltages is 0.
 - vi. Equation can be obtained by simplifying circuit based on principles of ideal op amp
- e. Non-Inverting Negative Feedback
- i. Signal into (+) terminal with feedback loop on negative terminal
 - ii. $V_{out} = V_{in}(1 + R_f/R_i)$
 - iii. Again, equation can be obtained by simplifying op amp based on basic principles
 - iv. Cannot be used as attenuator, only amplifier
- f. Unity Gain Buffer
- i. When $R_f = 0$ on a non-inverting feedback amp, it becomes a unity-gain buffer
 - ii. Input=Output, however input impedance is infinite and output impedance is almost zero, desirable effects for connecting gear
 - iii. Useful for plugging instruments into various devices
 - iv. Also can be used to drive long cables.
 - v. Cables have parasitic capacitance between hot and cold wires that acts as a low pass filter and lacks high frequencies
 - vi. Follows equation: $f_c = 1/2\pi Z_{\text{guitar}} C$

- vii. Zguitar can be controlled using unity gain buffer, eliminating the problem
- g. Gain versus Bandwidth
 - i. Non ideal op amps also have a capacitor inside of them and are prone to instability and oscillation
 - ii. Parasitic capacitances lead to positive feedback, causing high frequency limitations
 - iii. Negative feedback helps solve this, but lowers gain
 - iv. Lower the gain, greater the bandwidth
 - v. Systems should be able to amplify frequencies up to 20kHz
- h. Single Supply Biasing
 - i. Many pedal boxes etc are run on one 9V battery
 - ii. At bipolar operation, 0V input is 0V output as well
 - iii. In unipolar operation, 9V is connected to positive and negative is connected to ground
 - iv. Bias voltage must be applied so that negative frequencies can occur as well
 - v. With a 9V source, you will want the half supply voltage, or $V_{hs}=4.5V$
 - vi. To bias the circuit, you have to also connect the 9 volt source to the negative input and use a resistor divider to get V_{hs}
 - vii. Capacitors should be placed at all inputs and outputs to prevent DC voltage from flowing through circuit
- i. Capacitor Stuff
 - i. All op amps produce some inherent output DC voltage
 - ii. This means capacitors need to be placed to get rid of all DC voltage
 - iii. However, capacitors last the least time and can lead to problems in the circuit after a short time
 - iv. Also, introducing capacitors can lead to filtering and adds to impedance
 - v. Manufacturers try to use as few capacitors as possible
 - vi. There is often a ripple in the DC voltage source which can be heard in the signal, so bypass capacitors are placed in parallel with the source for any changes to go to ground.
 - vii. These can also be used with single supply biased amps
 - viii. Parasitic capacitance at the input can combine with the feedback resistor to create high frequency oscillations at the output
 - ix. Placing this in parallel with R_f will cause all high frequencies to feedback completely and are eliminated

III. MOAR OP AMPS

- a. Intro
 - i. Using these op amp designs, entire mixing systems with presamps, equalizer, panning, etc can be created
 - ii. Single supply biasing, bypass caps, coupling caps all can be added
 - iii. Devices can be connected together in series
- b. Input/Output Buffer
 - i. Adding these to the input/output can increase performance
 - ii. Input buffer creates a high input impedance
 - iii. Unity gain noninverting amp usually used
 - iv. Output buffer can be inverting or non inverting and used to give maximum current drive
- c. Mic Preamps

- i. Preamps need to satisfy impedance and balancing requirements
 - ii. Also need to provide high voltage gain since microphones get very low voltage levels
 - iii. Need high gain AND high input impedance
 - iv. High-Z
 - 1. 20K impedance and 20 mV output
 - 2. Unbalanced signal
 - v. Low-Z
 - 1. Impedance of 200 ohms and 2 mV output
 - 2. Balanced
 - 3. Can use another transformer or a differential amplifier
 - vi. See diagrams in book
 - d. Filters and Equalizers
 - i. Fixed low pass and high pass filters using op amps are common to get rid of excess noise/low freqs
 - ii. Variable filters important for equalizers, especially those using shelving filters
 - iii. See diagrams in book
 - iv. Common use of fixed filters is in crossovers for loudspeakers
 - v. Different drivers reproduce different frequencies.
 - vi. These can be active or passive
 - vii. Third order Butterworth crossovers address most of the design issues
 - viii. Sallen-Key, utilizes both positive and negative feedback
 - ix. Used as crossovers, no gain or Q or variable shit
 - x. Shelving Filters
 - 1. Most widely used filter
 - 2. Baxandall filter employs both high and low shelving at same time
 - xi. Graphic EQ
 - 1. Bank of parallel bandpass/bandstop
 - 2. Have fixed center frequency and adjustable boost/cut and Q
 - xii. Parametric EQ
 - 1. Adjustable boost, cut, center frequency, and Q
 - 2. Simpler than graphic EQ
 - e. Balanced Line Driver
 - i. Requires closest to ideal as possible op amps
 - ii. Converts unbalanced into balanced signal
 - iii. Simple and uses similar valued resistors
 - iv. Resistors must be matched with tight tolerance
 - v. Inverting amps have high input impedance
 - f. Oscillators
 - i. Positive feedback
 - ii. No input voltage
 - iii. Square wave, triangle wave, sine wave
 - iv. Square wave created by going from positive to negative rail
 - v. Lowpass filter added leads to sine wave
- IV. Tubes
 - a. Edisons light bulb: Filament inside of glass vacuum, which when currents passed through creates light. Gave off black soot though.
 - b. Positively charged plate added to collect electrons and soot, controlling flow of electrons

within the vacuum

- c. Second plate added as well to control the flow of electrons
- d. Second plate is **cathode**, first plate is **anode**, they make up the **diode**.
- e. Diode
 - i. Plate is positively charged in order for electrons to flow
 - ii. If you applied an AC voltage to the plate, current would only flow during the positive portion
- f. Half-Wave Rectification
 - i. Allows positive portions of AC waveform to pass through
 - ii. Plate is the input and cathode is the output
- g. Full wave rectification
 - i. Inverts negative portions of the input and combine them with the positive portions
 - ii. Can be made with multiple diodes, most often two diodes and a transformer
 - iii. Two plates shared in a tube
 - iv. Summed at the cathode
 - v. Center tapped transformer is used to feed the inverted and noninverted signals into the tube
 - vi. This tube is used to convert a 60Hz 120VAC signal into 250 V DC.
 - vii. The humps of the fully rectified signal are smoothed out to create a flat line using filters that get rid of the AC portion.
- h. Triode
 - i. Extra plate added, allowing constant positive charge for one plate, and extra plate to control the flow of electrons
 - ii. Type of screen called **control grid**
 - iii. If negative field is applied, electron flow towards positive plate will slow
 - iv. When grid at 0V, maximum flow, when no electrons flow, this is the cutoff.
 - v. By controlling grid voltage with an audio signal, you can get proportionally large changes in current flow with small changes in voltage
 - vi. Often multiple triodes will be used